



Faculty of Engineering & Technology Electrical & Computer
Engineering Department
ENEE2103
CIRCUITS AND ELECTRONICS LABORATORY
Prelab IV

Name and ID : Raghad Afaghani - 1192423

Section : 2

Instructor : Dr. Mohammad Al Ju'beh

Teacher Assistant : Eng. Bilal Ismail

Date : 28.5.2023

1.Characteristic of an n-channel JFET:

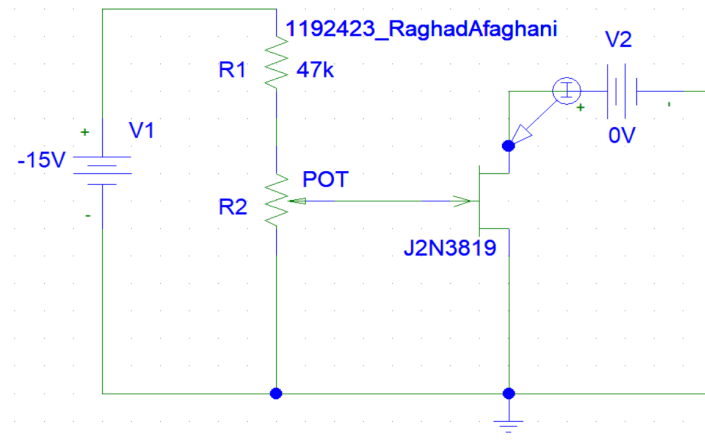


Figure 1. Characteristic of an n-channel JFET

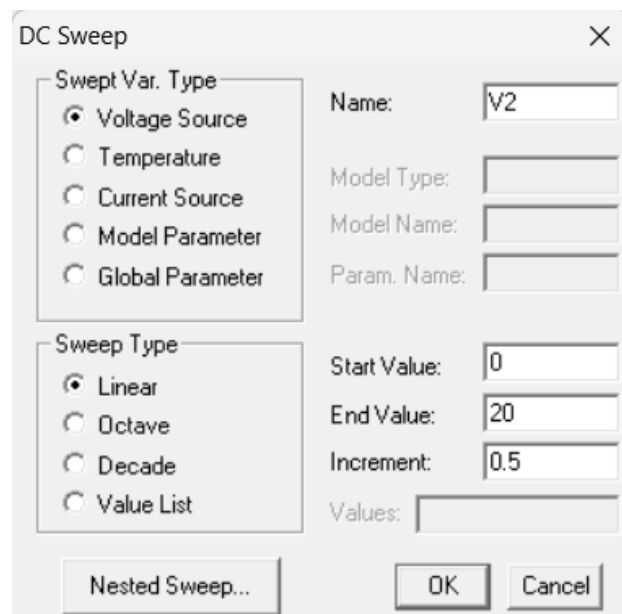


Figure 2. DC Sweep

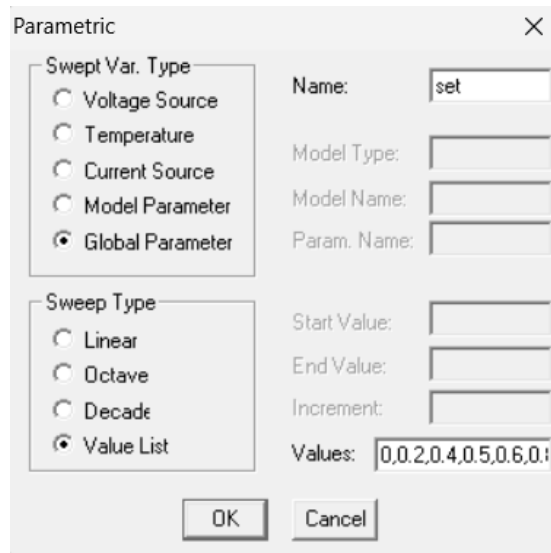


Figure 3. Parametric Values

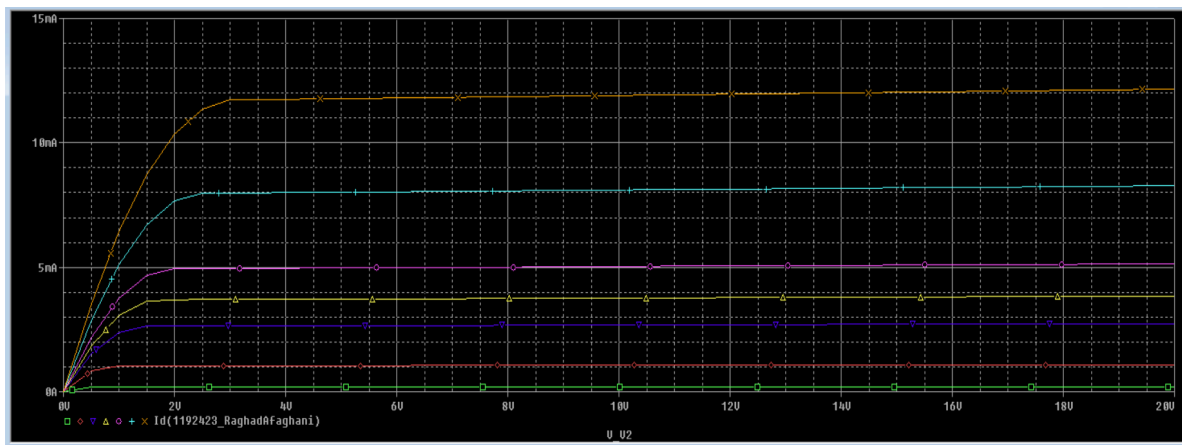


Figure 4. IDS as function of VDS

Questions:

- From your graph, above which values of V_{DS} is I_D almost unaffected by V_{DS} when $V_{GS}=0$?

When $V_{GS}=0$ and $V_{DS}=2V$, the values of I_D remain largely unchanged.

- For a given value of V_{DS} , (say 10 V), do equal changes of V_{GS} cause equal changes of I_D ?

Junction between the source and gate Reverse bias junction so the value of I_d is too small close to zero

- Can you measure I_G or is it too small?

It is not possible to measure I_G as it is an extremely small quantity.

- From your graph, estimate the change in I_D for 0.5 change in V_{GS} when $V_{DS}=10$ V, and V_{GS} -1.0 V, then find the transconductance of the transistor(g_m).

$$\text{Transconductance} = g_m = (\text{change in } I_D) / (\text{change in } V_{GS}) = \frac{2 \times I_{DS}}{V_{DS}} \times \left(1 - \frac{V_{GS}}{V_{DS}}\right) =$$

$$\frac{2 \times 3.5459}{1.5} \times \left(1 - \frac{-1}{1.5}\right) = 7.87978.$$

2.Common Drain Amplifier Circuit

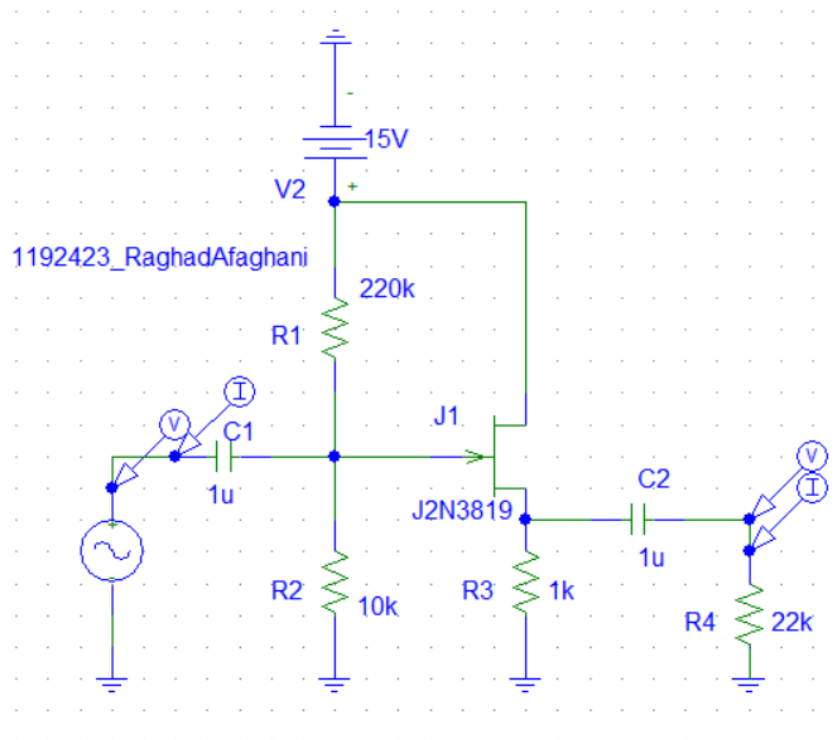


Figure 5. Common Drain Amplifier Circuit

1. Conduct a bias point analysis and measure the DC voltages of VG and VS.


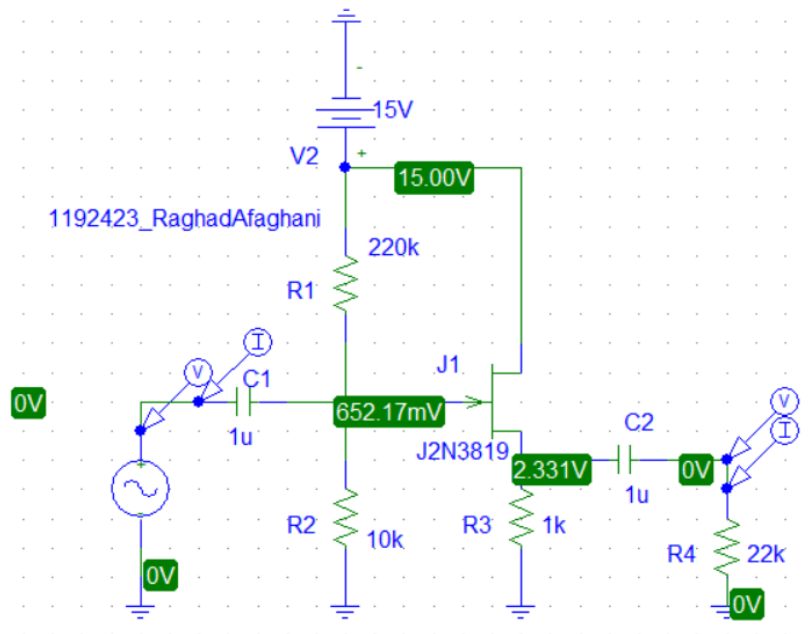
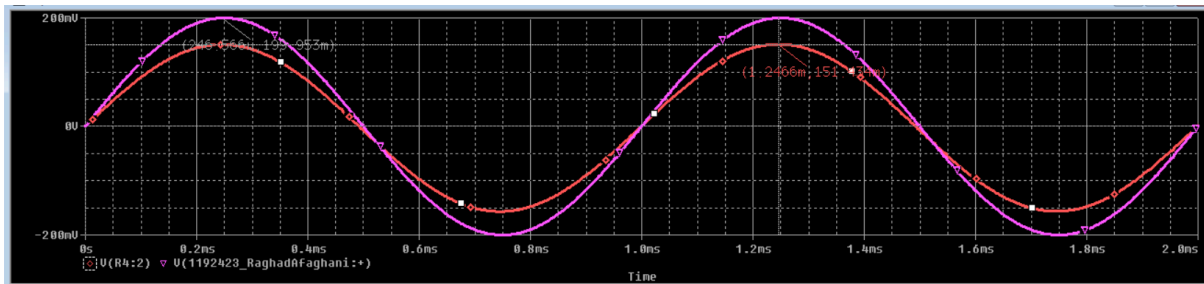


Figure 6. DC voltages of VG&VS

- The simulation result shows that V_g is 652.17mV and V_s is 2.331V.
- To calculate V_g using the voltage divider rule:
 - $$\frac{R_2}{R_2+R_1} * V_2 = \frac{10k}{10k+220k} * 15 = 652.5mV.$$

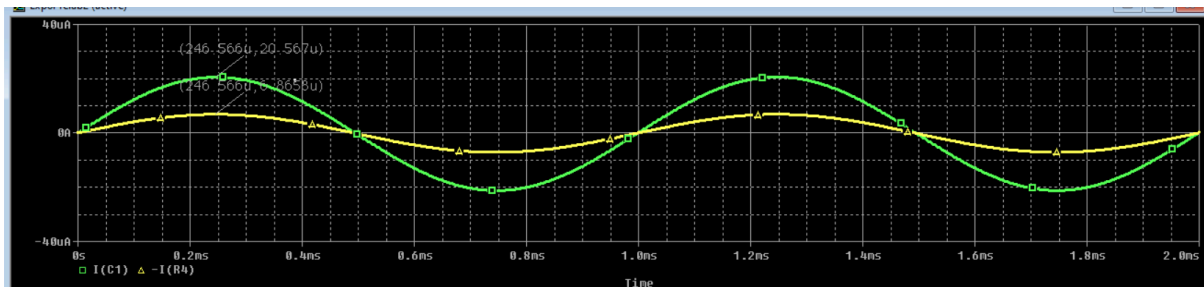2. Apply a 0.4-volt peak-to-peak input with a frequency of 1 kHz from the generator, and observe the corresponding input and output currents and voltages.



3. To calculate the voltage gain and phase shift between the input and output voltage:

- The voltage gain (A_v) is given by $A_v = V_{out} / V_{in} = 151.434 \text{ mV} / 199.953 \text{ mV} = 0.75735$.
- The current gain (A_I) is given by $A_I = I_{out} / I_{in} = 6.8658 \text{ u} / 20.567 \text{ u} = 0.333826$.
- The phase shift is given by $\Delta\phi = \frac{T_{\Delta pp} \times 360}{\text{period}} = \frac{(1.2506m - 12506m) \times 360^\circ}{1.0m} = 0^\circ$

4. To determine the values of Z_{in} and Z_{out} using the appropriate voltages and currents at the specified locations in the previous figure:

- The value of I_{in} is 20.567 μA and the value of I_{out} is 6.8658 μA .
- Z_{in} is calculated as $V_{in} / I_{in} = 199.953 \text{ mV} / 20.567 \text{ uA} = 9.722030 \text{ k}\Omega$.
- Z_{out} is calculated as $V_{out} / I_{out} = 151.434 \text{ mV} / 6.8658 \text{ uA} = 22.056279 \text{ k}\Omega$.

3.Constant Current Source

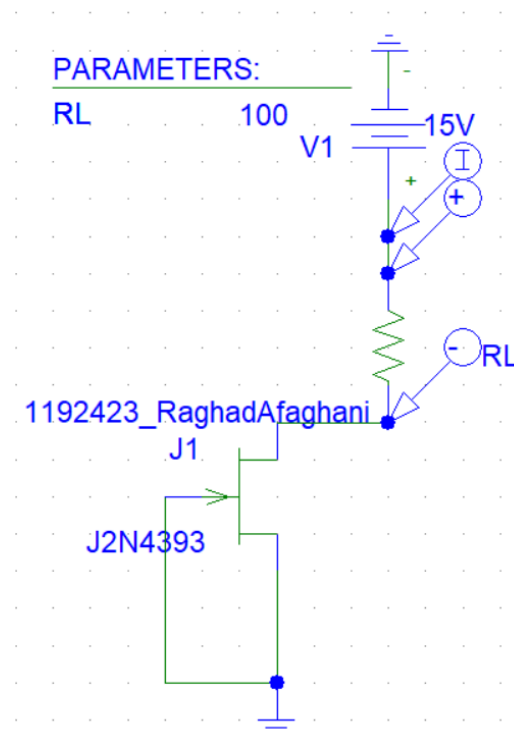


Figure 7. Constant Current Source

1. Conduct a DC sweep for the value of RL within the specified range.


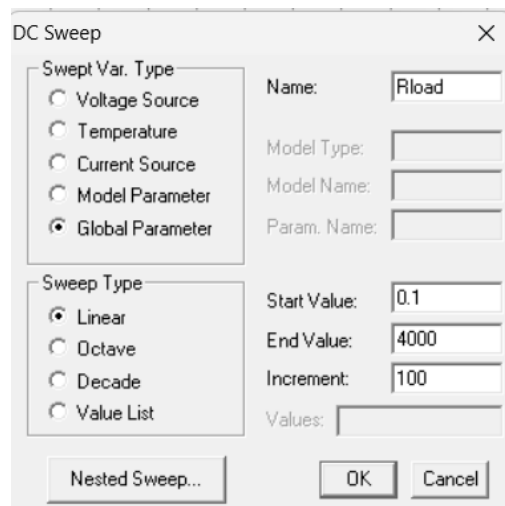
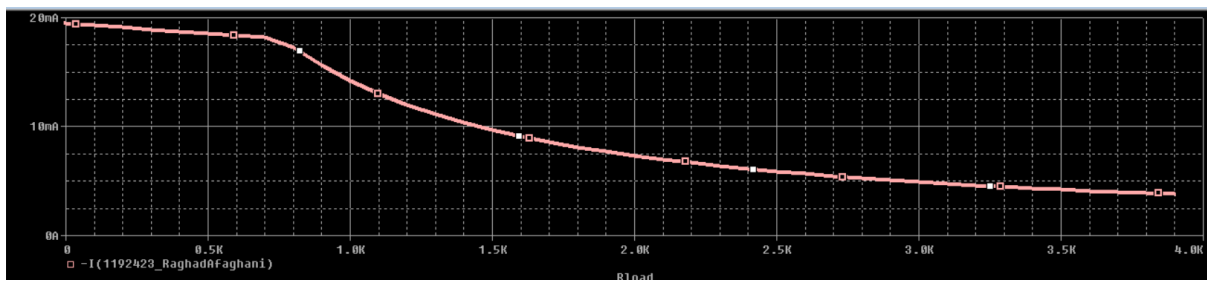


Figure 8. DC sweep for RL Value

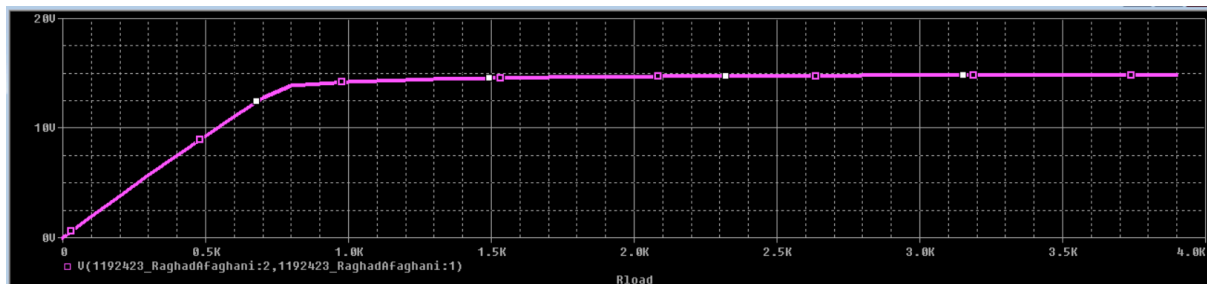2.The plots show the current ID and voltage VL across the resistor RL.



3.Display the voltage VL across the resistor and the current IDS.

$R_L(K\Omega)$	$V_L(V)$	$I_D(mA)$
0.1	1.9323	19.323
0.22	4.1959	19.081
0.33	6.2503	18.876
0.47	8.7172	18.607
0.56	10.374	18.444
1	14.224	14.218
1.5	14.537	9.690
2	14.666	7.3228
3	14.785	4.9282

Table 1. V_L across the resistor R_L and I_D