



Faculty of Engineering & Technology Electrical & Computer
Engineering Department
ENEE2103
CIRCUITS AND ELECTRONICS LABORATORY
Prelab V

Name and ID : Raghad Afaghani - 1192423

Section : 2

Instructor : Dr. Mohammad Al Ju'beh

Teacher Assistant : Eng. Bilal Ismail

Date : 5.6.2023

Adding Application

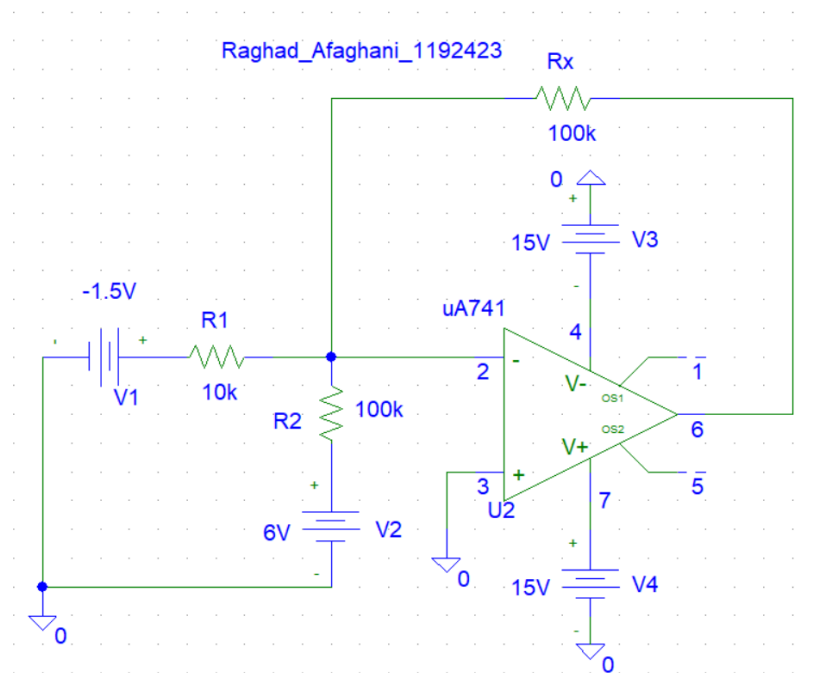


Figure 1. Adding Circuit


Input voltage		Output voltage	
V_1	V_2	V_o	Calculated voltage
0.5	2	-6.991	-7
0.4	3	-6.991	-7
0.3	4	-6.991	-7
-0.9	4	5.008	5
-1.1	5	6.008	6
-1.5	6	9.008	9

Table 1. Values of V_o


Based on the previous results, the circuit behaves as an inverting adder; thus,

$$V_o = - \left(\frac{R_3}{R_1} V_1 + \frac{R_3}{R_2} V_2 \right).$$

Voltage Follower Application:

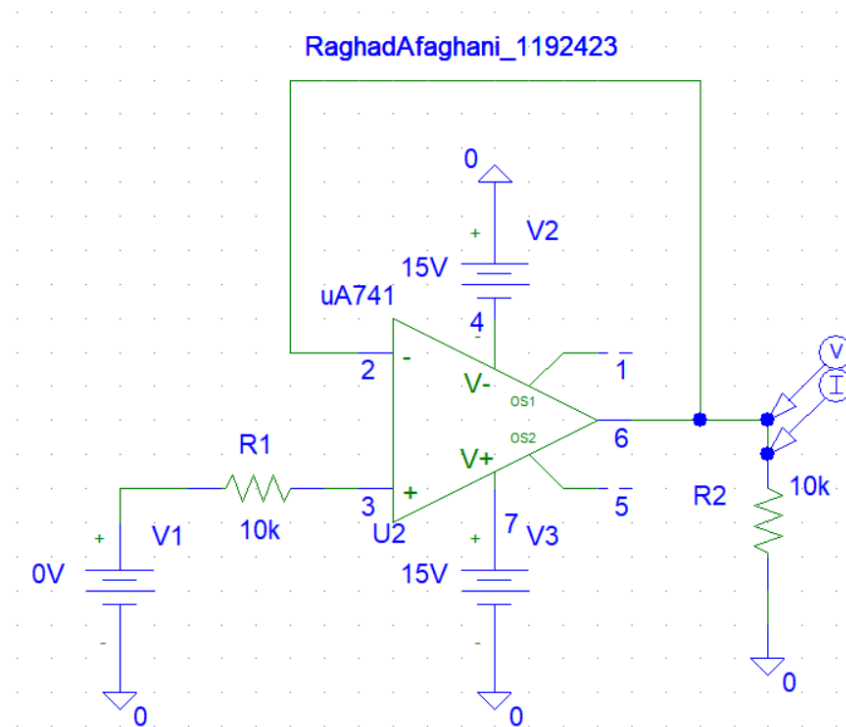


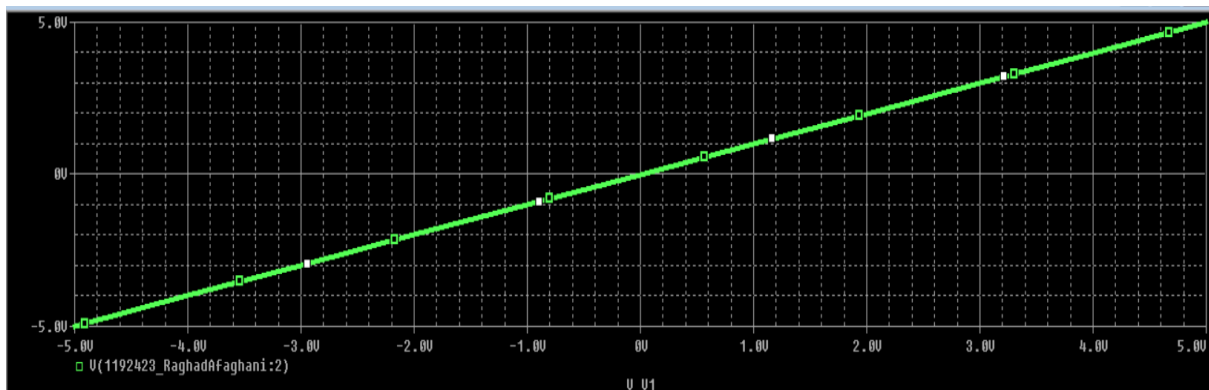Perform DC sweep For DC voltage source V_1 , plot V_O and observe the relationship





The previous simulation demonstrated that there is a linear relationship between V_I and V_O , indicating that the circuit functions as a buffer circuit.

Plot I_O

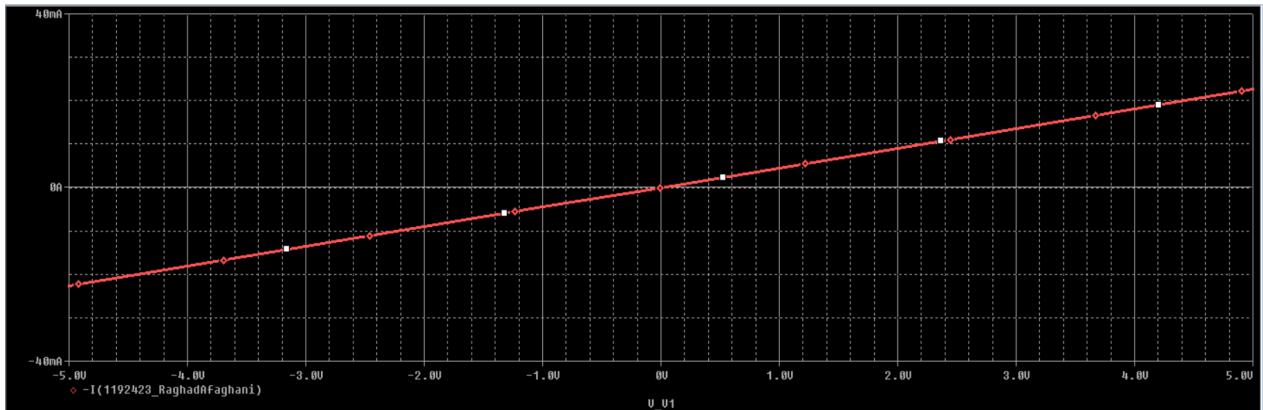

The behavior of I_O is depicted in the preceding graph, which can be expressed mathematically as $I_O = \frac{V_O}{R}$.

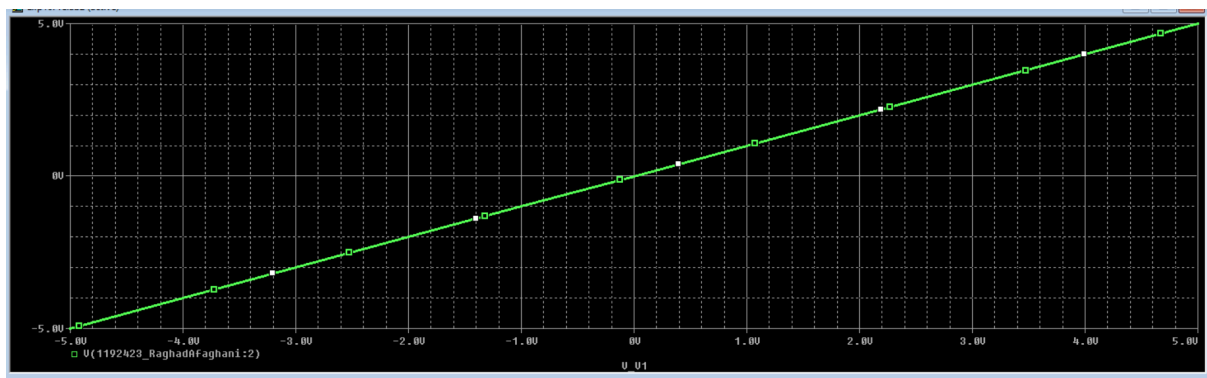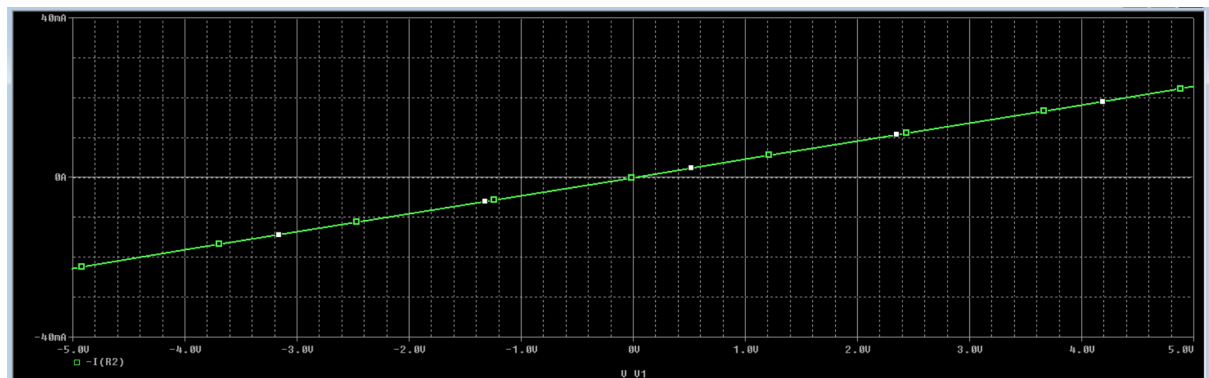When the 220-ohm resistor replaced by 10 k ohm:



From the preceding figures, it can be observed that the value of V_O remains unaffected by variations in the value of R . Nevertheless, when a higher resistor value of $R=10\text{ k ohm}$ is employed, I_O is diminished, indicating an inverse relationship between I_O and R .

Comparator Application:



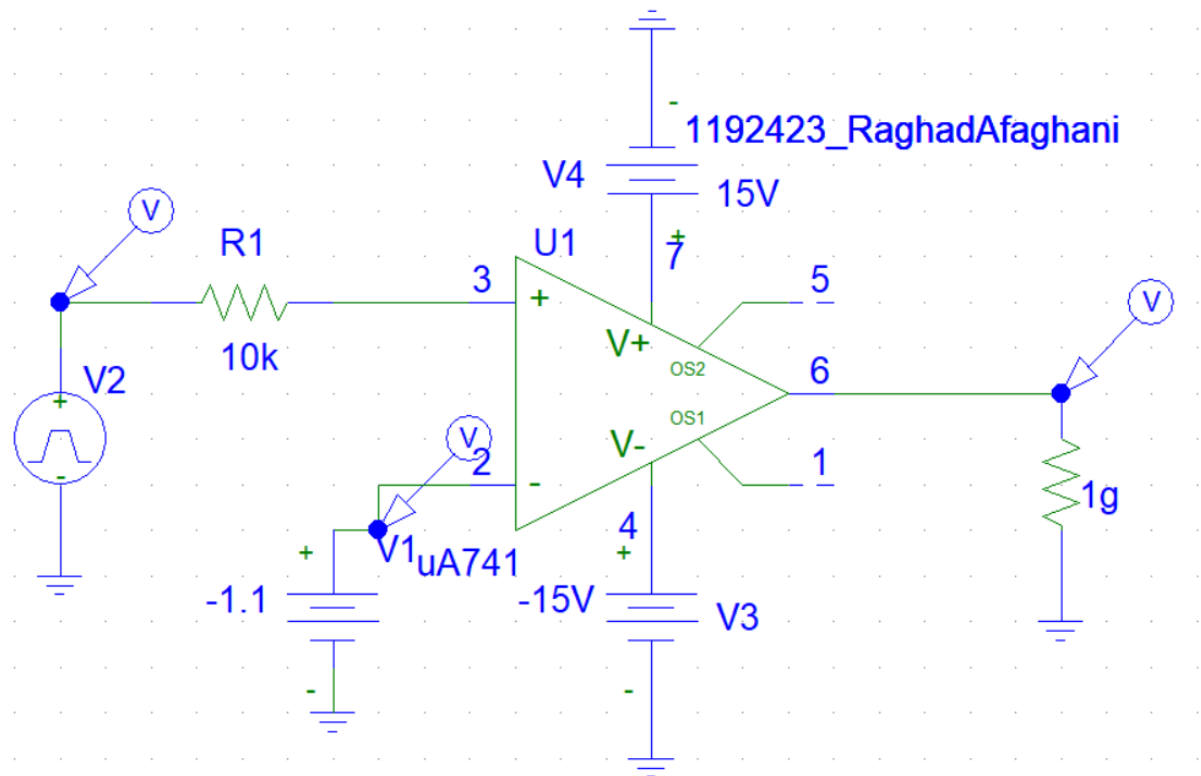


Figure 3. Comparator Circuit


When $V1 = 0V$

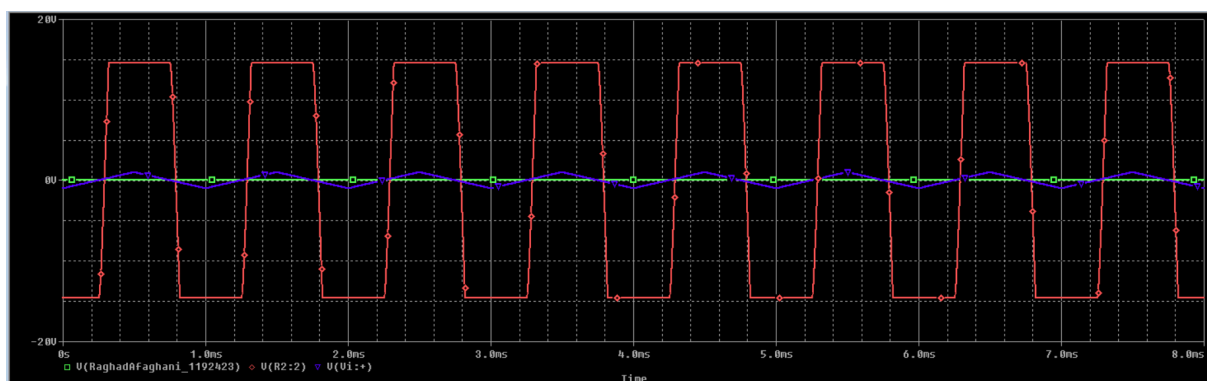

When $V_1 = 1.1V$

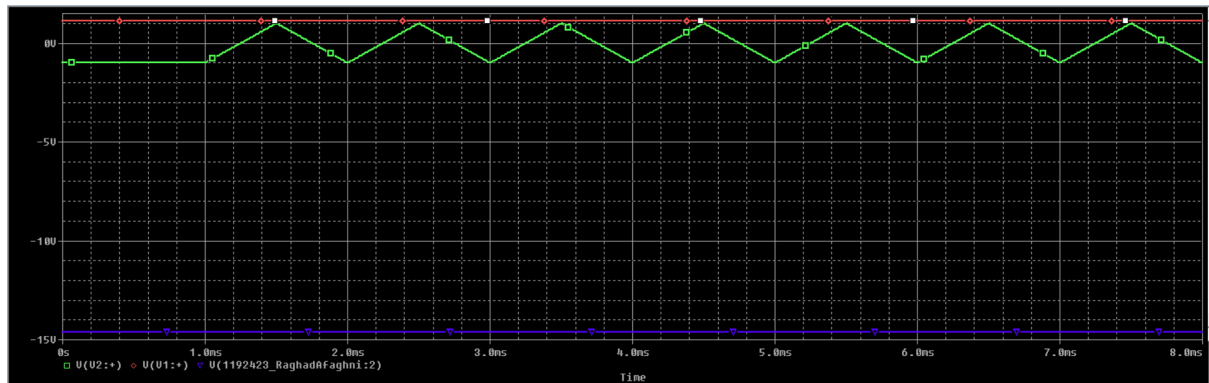

When $V_1 = -1.1V$

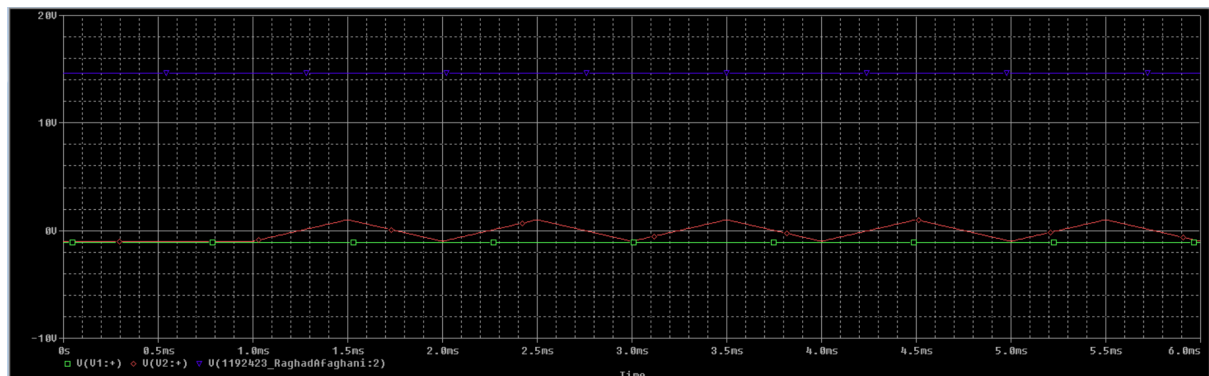

Based on the preceding graphs, we can infer the following:

- If the input voltage surpasses the reference voltage, the output voltage will rise to a positive saturation level of 15 volts.
- If the input voltage falls below the reference voltage, the output voltage will decline to a negative saturation level of -15 volts.

Integrator and Differentiator:


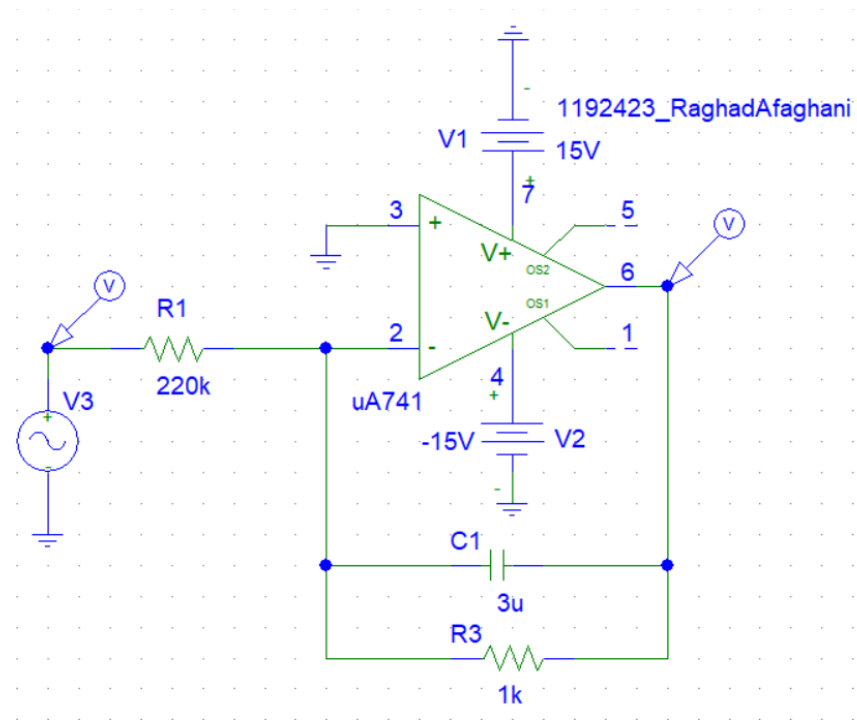
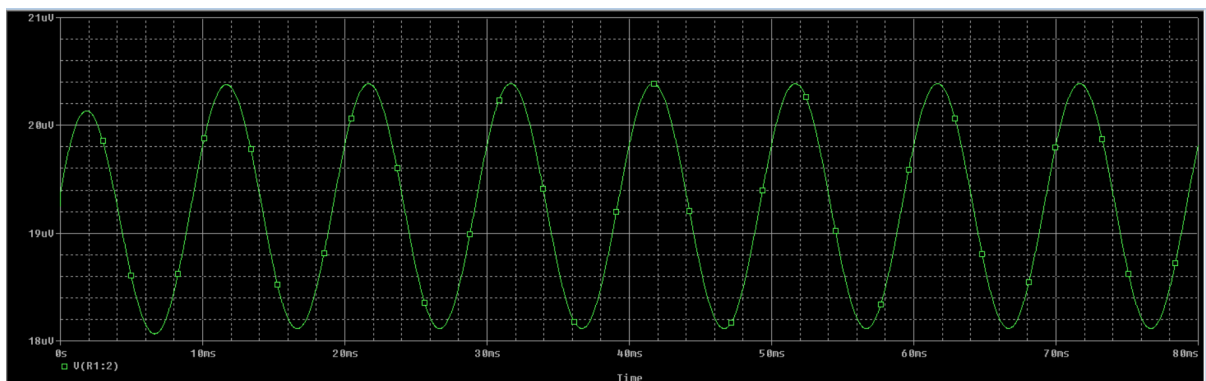


Figure 4. Integrator Circuit

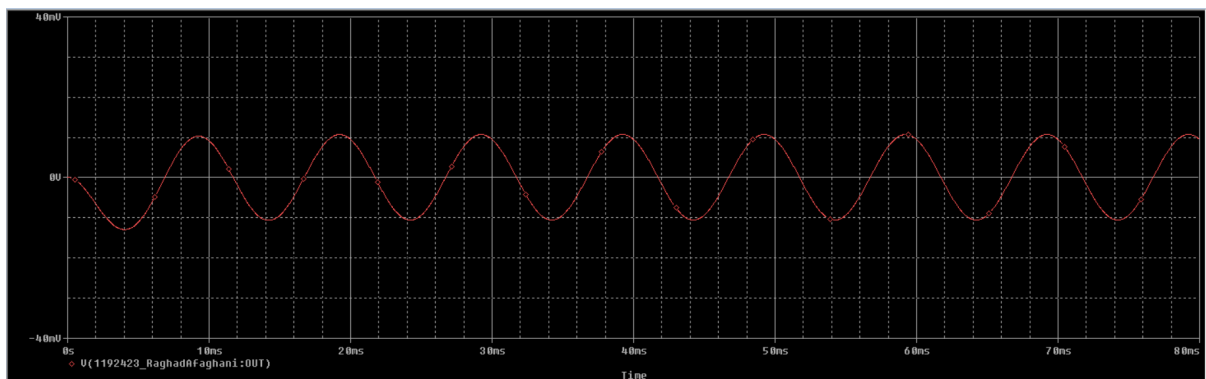

Differentiator:


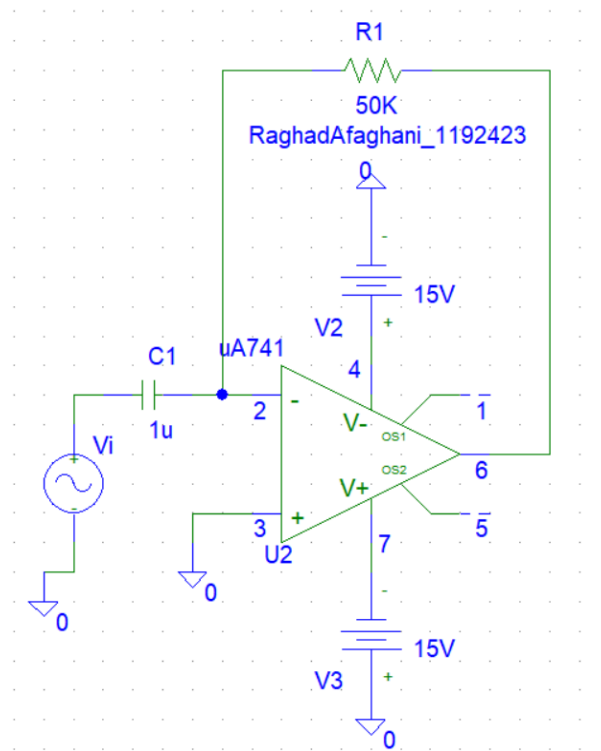


Figure 5. Differential Circuit

Plot of V_o and V_i

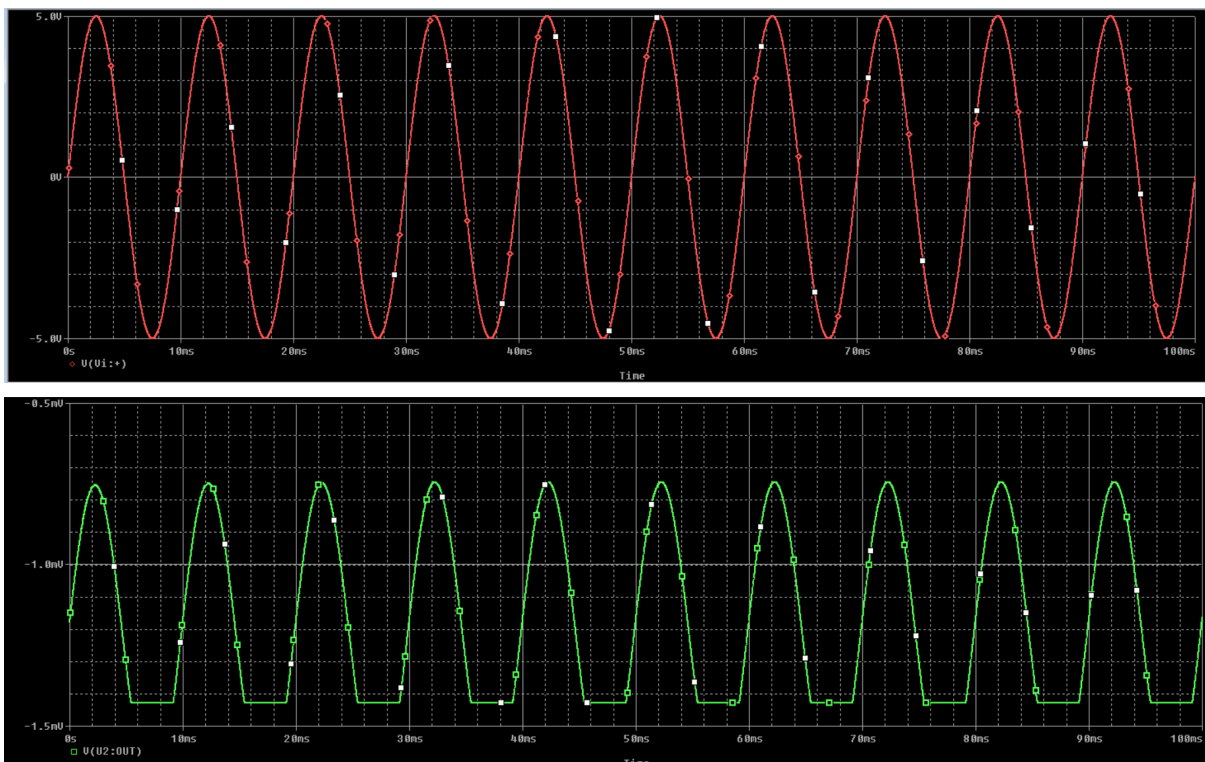

Investigate the effect of adding hysteresis:


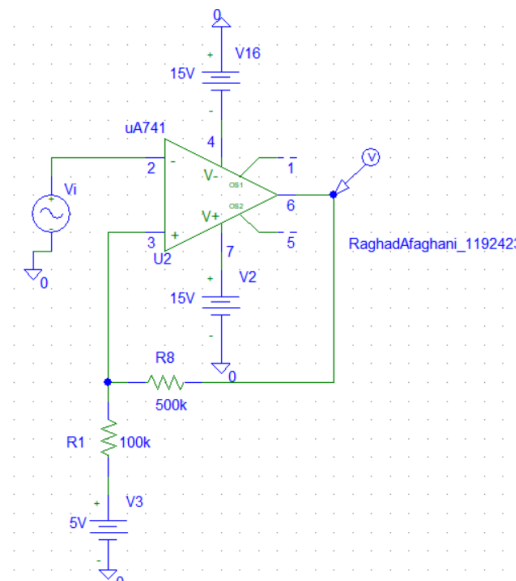


Figure 6. Effect of Adding Hysteresis

Plot the Vo and Vi

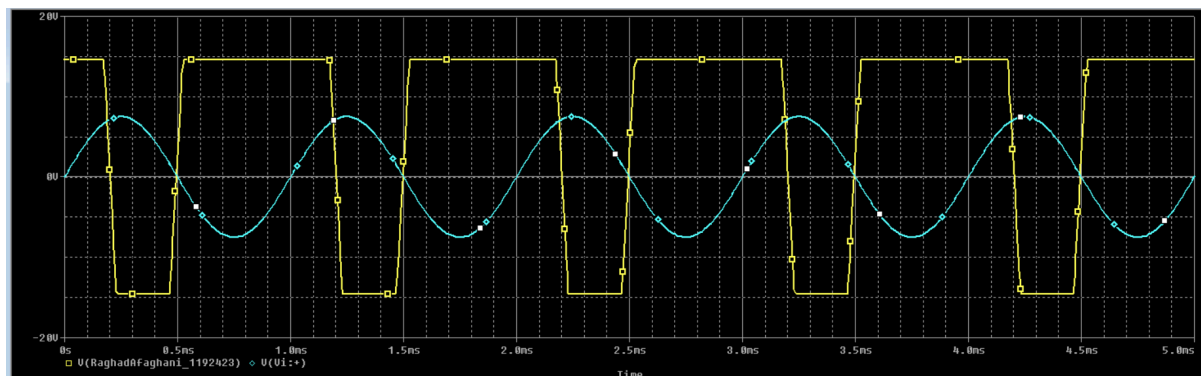

- To determine the levels of $V_i(t)$ where $V_o(t)$ transitions from low to high and high to low, we need to analyze the Schmitt trigger comparator circuit. The output voltage of the circuit is either $+V_{sat}$ or $-V_{sat}$, depending on the voltages at V_+ and V_- .
- Assuming $V_o = +V_{sat} = V_{cc} - 2 = 15 - 2 = 13$ V, we can calculate V_+ as follows:

$$V_+ = \frac{R_2}{R_2 + R_1} * V_{sat} + \frac{R_1}{R_2 + R_1} * V(2) = \frac{100k}{(100k + 500k)} * 13 + \frac{500k}{(100k + 500k)} * 5 = 6.3333 \text{ V}.$$
- Therefore, when V_{in} is less than the upper threshold voltage of $V_+ = 6.3333$ V, V_o will be $+V_{sat} = 13$ V.
- Assuming $V_o = -V_{sat} = -V_{cc} + 2 = -15 + 2 = -13$ V, we can calculate V_+ as follows:

$$V_+ = \frac{R_2}{R_2 + R_1} * (-V_{sat}) + \frac{R_1}{R_2 + R_1} * V(2) = \frac{100k}{(100k + 500k)} * (-13) + \frac{500k}{(100k + 500k)} * 5 = 2 \text{ V}.$$

- Therefore, when V_{in} is greater than the lower threshold voltage of $V_- = 2\text{ V}$, V_o will be $-V_{sat} = -13\text{ V}$.

- Thus, the circuit has hysteresis, and the hysteresis voltage can be calculated as follows:

Hysteresis voltage = Upper threshold voltage - Lower threshold voltage = $6.3333\text{ V} - 2\text{ V} = 4.3333\text{ V}$.