



Faculty of Engineering & Technology Electrical & Computer
Engineering Department
ENEE2103
CIRCUITS AND ELECTRONICS LABORATORY
PreLab 1

Name and ID : Raghad Afaghani - 1192423

Section : 2

Instructor : Dr. Mohammad Al Ju'beh

Teacher Assistant : Eng. Bilal Ismail

Date : 6.4.2023

Part 1 : KVL,KCL

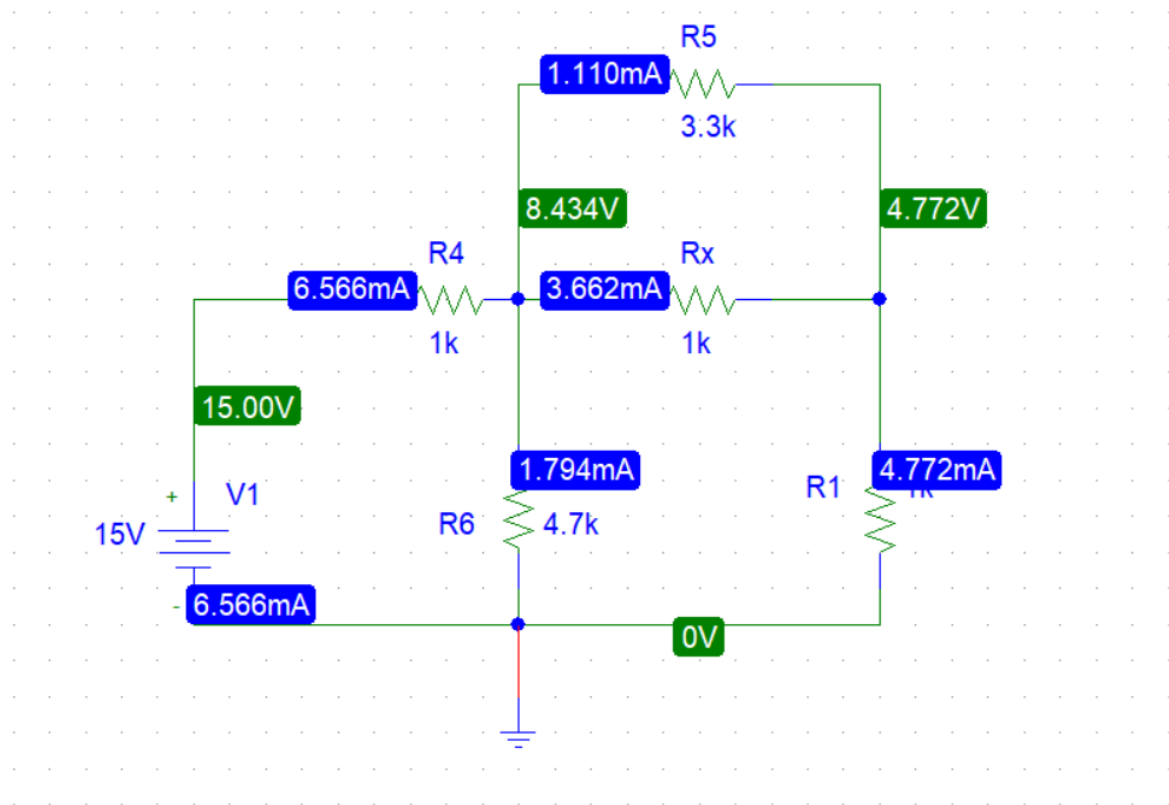


Figure 1: KCL and KVL Circuit

Vs		R1		R4		R5		R6		Rx	
		V1	I1	V4	I4	V5	I5	V6	I6	Vx	Ix
15 V	Rx = 1k	4.772 V	4.772mA	15V	6.566mA	3.662V	1.11mA	8.4318V	1.794mA	3.662V	3.662mA

Table1: KCL and KVL Circuit Values

Part 2 : Voltage and Current Division

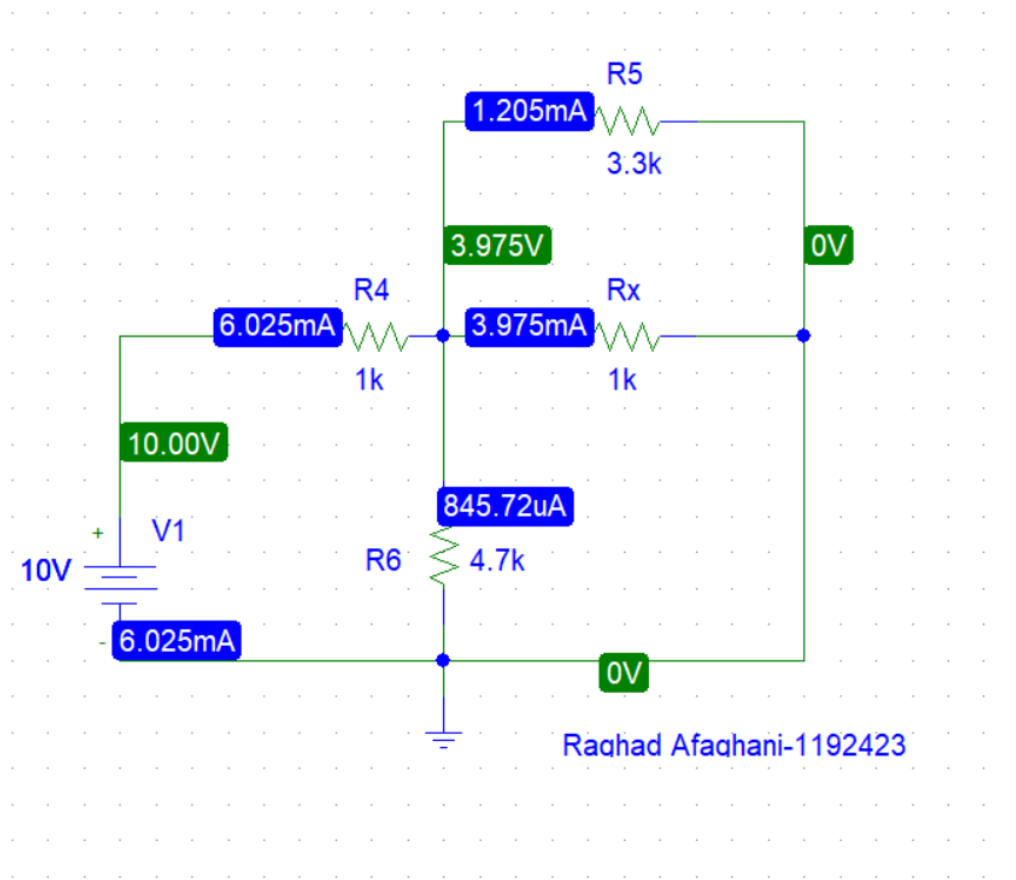


Figure 2: Current division Circuit

Vs (volt)	Pot.	I4	I5	I6	Ix
10	Rx = 1k	6.025 mA	1.205 mA	845.72 uA	3.975 mA

Table2: Current Division Circuit Values

Part 3 : Superposition

- When set the source V_{s1} to 5 volts and V_{s2} to 10 volts as shown in Figure 3:

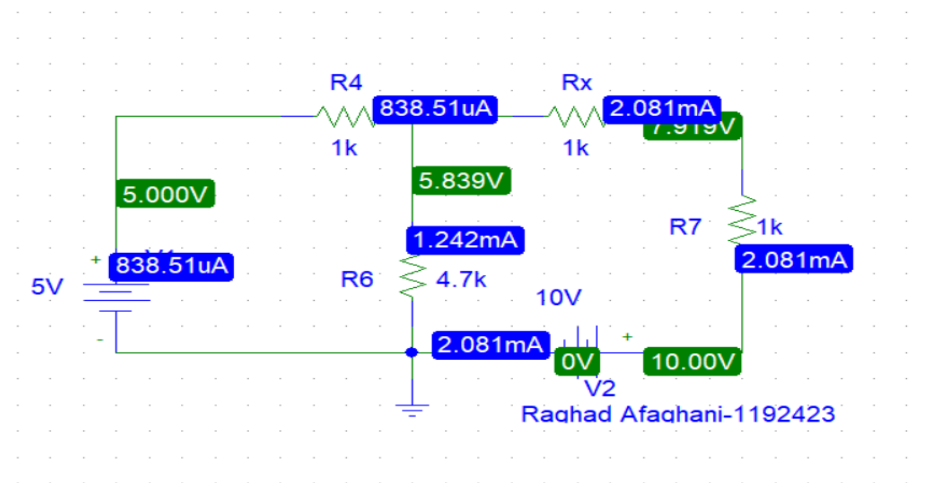


Figure 3: $V_{s1} = 5V$ and $V_{s2} = 10V$

- When set the source V_{s1} to 0 volts and V_{s2} to 10 volts as shown in Figure 4:

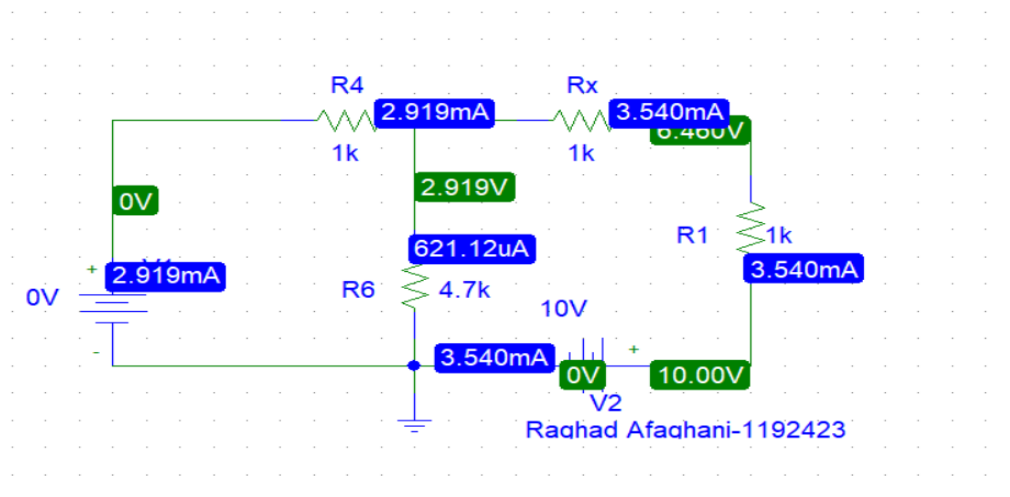


Figure 4: $V_{s1} = 0V$ and $V_{s2} = 10V$

- When set the source V_{s1} to 5 volts and V_{s2} to 0 volts as shown in Figure 5:

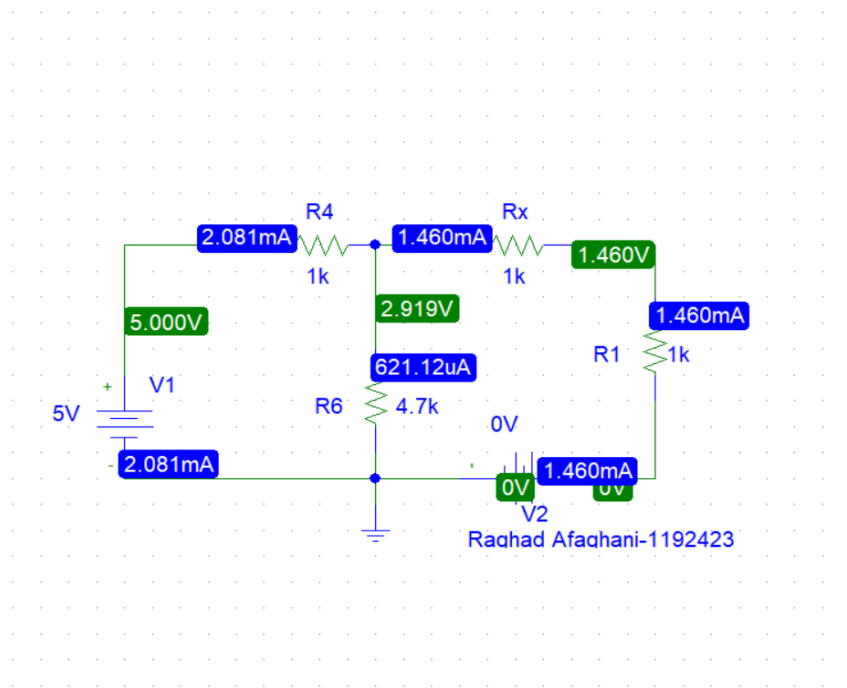


Figure 5: $V_{s1} = 5V$ and $V_{s2} = 0V$

$V_{s1}(\text{volt})$	$V_{s2}(\text{volt})$	$V_6(\text{volt})$	$I_6(\text{mA})$
5	10	5.839 V	1.242 mA
0	10	2.919 V	621.12 uA
5	0	2.919 V	621.12 uA

Table 3: Superposition Circuit Values

Part 4 : Thevenin and Norton equivalent circuits:

1. If V_{s1} is adjusted to 5 volts and V_{s2} to 10 volts, with R_6 set to 1K ohm, the voltage across R_1 can be calculated as $7-10=-3V$.

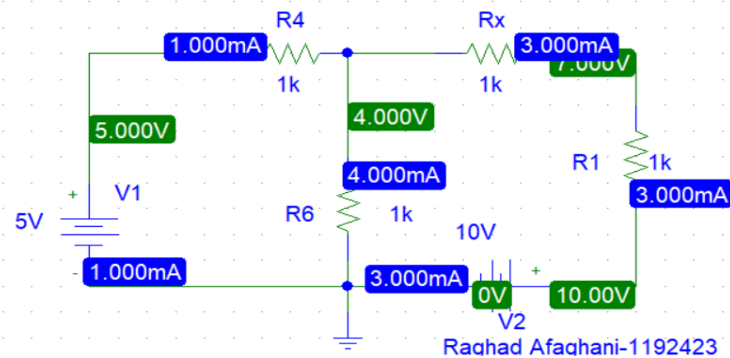


Figure 6: To find the value of voltage across R_1

2. In order to find V_{oc} “open circuit voltage” = V_{th} : current source “IDC” was inserted between nodes a and b with a value of 0 A. As a result, V_{oc} was calculated to be equal to $V_{th} = 2.5 - 10 = -7.5V$.

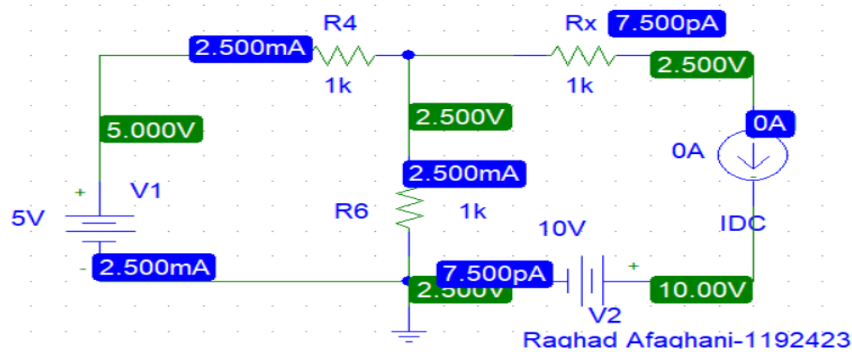


Figure 7: To find the value of open circuit voltage

- find the current in the short circuit (I_{sc}): $I_{sc} = -5 \text{ mA}$. (By making a short circuit between nodes a and b).

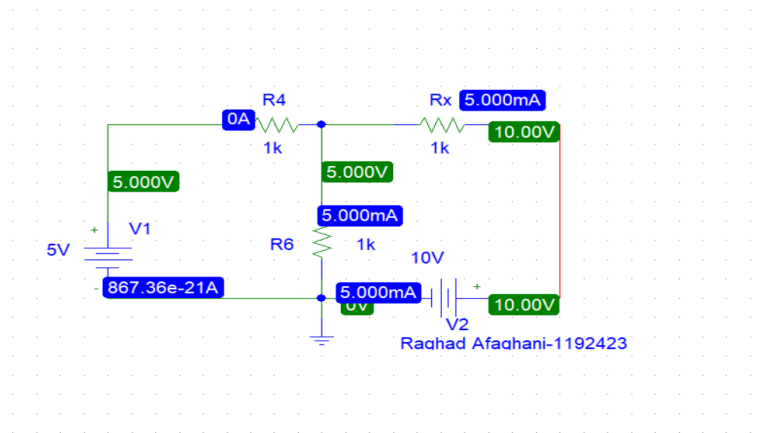


Figure 8: To find the value of I_{sc}

- The value of R_{th} , which is equivalent to R_{ab} and can be calculated as V_{th}/I_{sc} or V_{oc}/I_{norton} , is 1.5K ohm when we substitute the values of -7.5V for V_{oc} and -5mA for I_{sc} .

Another way to obtain the value of R_{th} is by replaced V_{s1} and V_{s2} by short circuit and $R1$ with open circuit then find the equivalent register:

- ❖ $R1$, $R6$ in parallel, then $R_{eq1} = 0.5 \text{ K ohm}$.
- ❖ R_{eq1} , Rx in series, then $R_{eq} = R_{th} = 1.5 \text{ k ohm}$.

- When connecting the voltage source in a series with the potentiometer's variable resistance(V_{R1}), and connecting the resistance $R1$ across the terminals a-b:

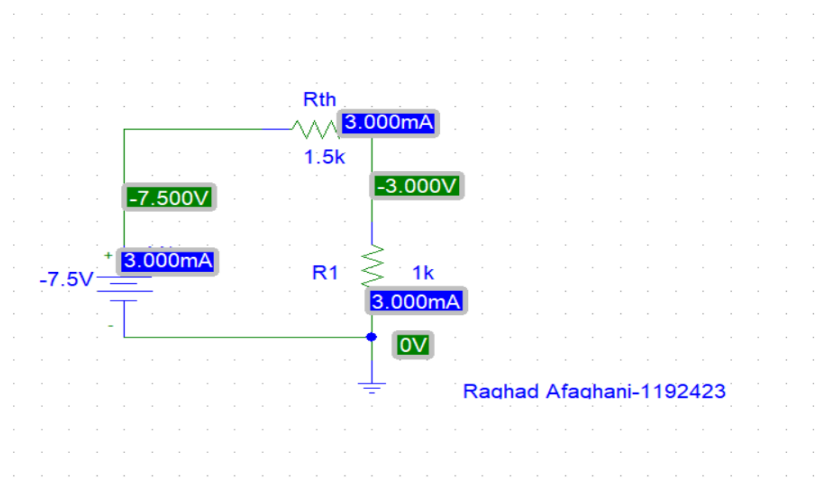


Figure 9: when connect voltage source in series with the R_{th}

6. As shown from Figure 9 , the voltage across R1, which is also equal to V_{R1} , is -3 volts (-3 - 0), this value is equal to the value measured in step 1.